

ASSIGNMENT -1

Soundarya*

Write the Boolean Expression for the result of the Logic Circuit as shown below :

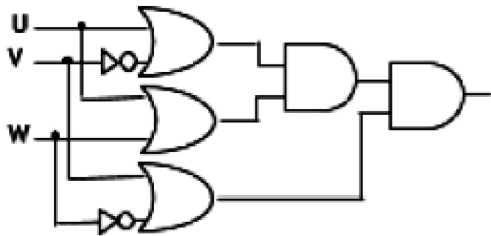


Fig. 0. LOGIC CIRCUIT

$$F = U(V + W!)$$

<https://github.com/soundaryanaru/FWC-assignments>